

L11: Major/Minor FSMs




Acknowledgements:


Materials in this lecture are courtesy of the following sources and are used with permission.

Rex Min


- Consider the following abstract FSM:

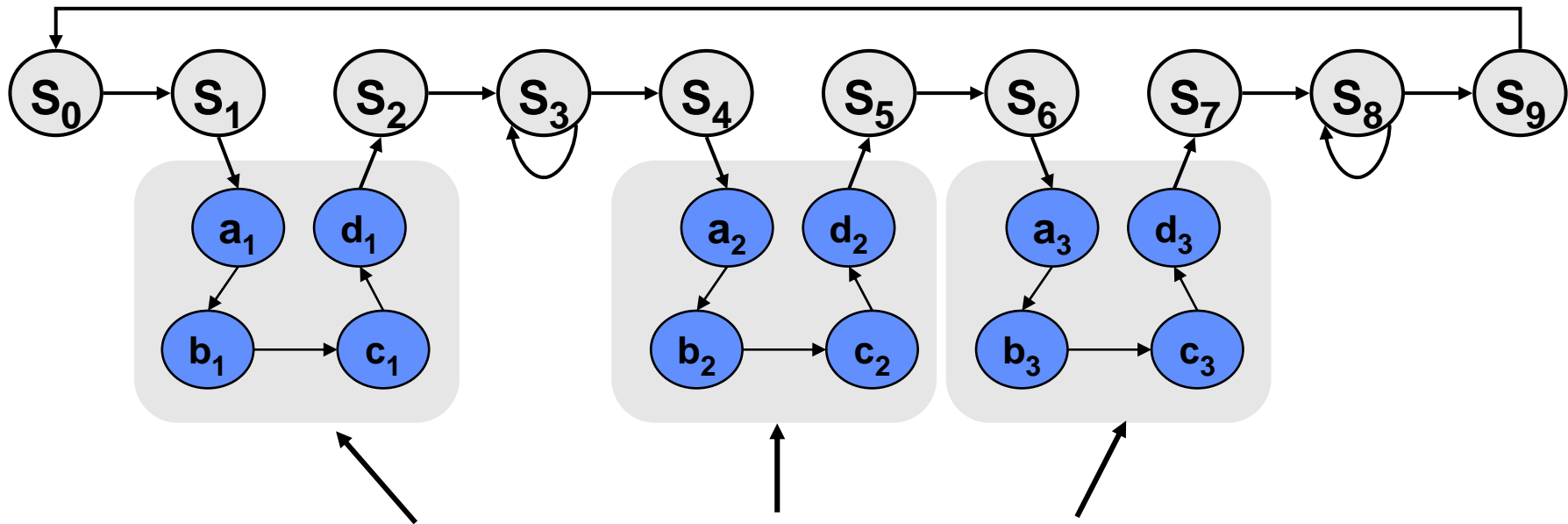

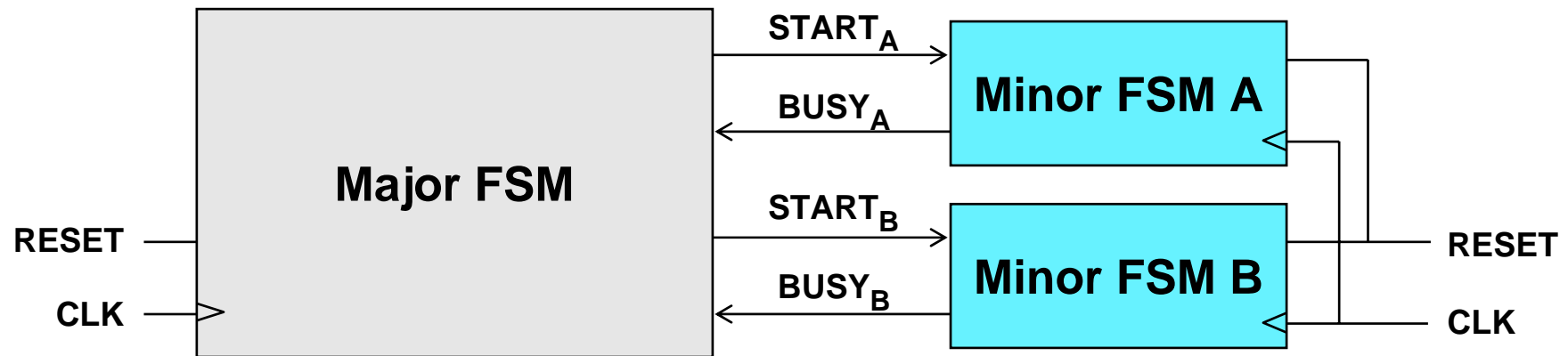- Suppose that each set of states $a_x \dots d_x$ is a “sub-FSM” that produces exactly the same outputs.
- Can we simplify the FSM by removing equivalent states?
No! The outputs may be the same, but the next-state transitions are not.
- This situation closely resembles a **procedure call** or **function call** in software...how can we apply this concept to FSMs?




- Subtasks are encapsulated in **minor FSMs** with common reset and clock
- Simple communication abstraction:
 - START: tells the minor FSM to begin operation (the call)
 - BUSY: tells the major FSM whether the minor is done (the return)
- The major/minor abstraction is great for...
 - Modular designs (*a/ways* a good thing)
 - Tasks that occur often but in different contexts
 - Tasks that require a variable/unknown period of time
 - Event-driven systems


 


1. Wait until the minor FSM is ready


2. Trigger the minor FSM (and make sure it's started)

3. Wait until the minor FSM is done

 

 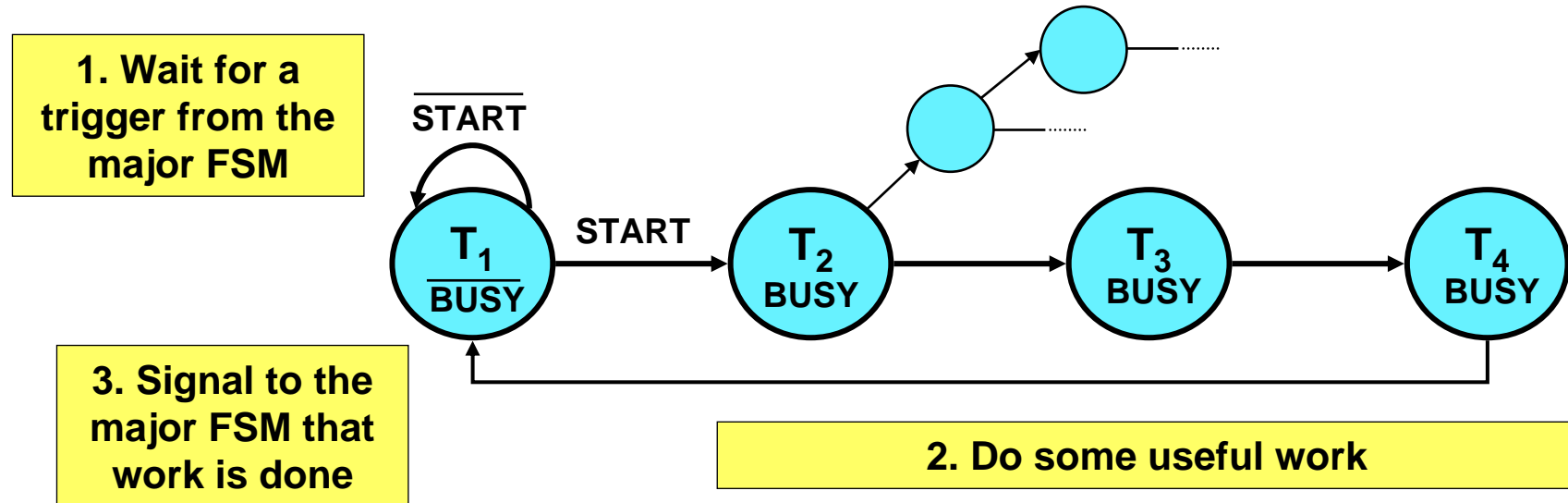


 Good idea: de-assert BUSY one cycle early



Bad idea #1:

T_4 may not immediately return to T_1

 

Bad idea #2:

BUSY never asserts!

